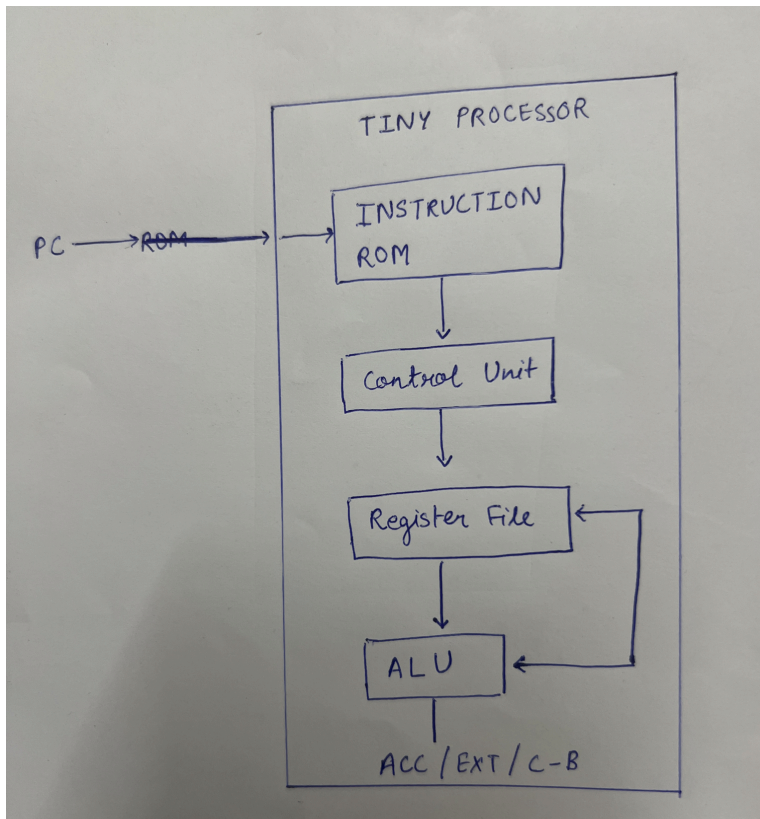


# Tiny Processor

## Block Diagram:



## Simulation code:

```
module Instruction_ROM (
    input [3:0] PC,
    output reg [7:0] instruction
);
    reg [7:0] ROM [0:15];

    always @(*) begin
        instruction = ROM[PC];
    end
endmodule

module Control_Unit (
    input [7:0] instruction,
    output reg [3:0] opcode,
    output reg [3:0] reg_addr
);
    always @(*) begin
        opcode = instruction[7:4];
        reg_addr = instruction[3:0];
    end
end
```

```

endmodule

module Register_File (
    input clk,
    input we,
    input [3:0] read_addr,
    input [3:0] write_addr,
    input [7:0] data_in,
    output reg [7:0] data_out
);
    reg [7:0] regs [0:15];

    always @(posedge clk) begin
        if (we)
            regs[write_addr] <= data_in;
        end

    always @(*) begin
        data_out = regs[read_addr];
    end
endmodule

```

```

module ALU (
    input [3:0] opcode,
    input [7:0] ACC,
    input [7:0] RegIn,
    output reg [7:0] result,
    output reg C_B,
    output reg [7:0] EXT
);
    always @(*) begin
        C_B = 0;
        EXT = 0;
        case (opcode)
            4'b0001: {C_B, result} = ACC + RegIn; // ADD
            4'b0010: {C_B, result} = ACC - RegIn; // SUB
            4'b0011: {EXT, result} = ACC * RegIn; // MUL
            4'b0101: result = ACC & RegIn; // AND
            4'b0110: result = ACC ^ RegIn; // XRA
            4'b0111: begin // CMP
                C_B = (ACC < RegIn) ? 1 : 0;
            end
            default: result = ACC;
        endcase
    end
endmodule

```

```

module TinyProcessor (
    input clk,

```

```

input reset
);
reg [3:0] PC;
reg [7:0] ACC, EXT;
reg C_B;

wire [7:0] instruction;
wire [3:0] opcode, reg_addr;
wire [7:0] reg_data;
wire [7:0] alu_out, ext_out;
wire alu_CB;

reg write_enable;
reg [3:0] write_reg;

Instruction_ROM rom(PC, instruction);
Control_Unit cu(instruction, opcode, reg_addr);
Register_File rf(clk, write_enable, reg_addr, write_reg, ACC, reg_data);
ALU alu(opcode, ACC, reg_data, alu_out, alu_CB, ext_out);

always @(posedge clk or posedge reset) begin
    if (reset) begin
        PC <= 0;
        ACC <= 0;
        EXT <= 0;
        C_B <= 0;
    end else begin
        write_enable <= 0;
        case (opcode)
            4'b0000: begin
                case (instruction[3:0])
                    4'b0000: ; // NOP
                    4'b0001: ACC <= ACC << 1; // LSL
                    4'b0010: ACC <= ACC >> 1; // LSR
                    4'b0011: ACC <= {ACC[0], ACC[7:1]}; // CIR
                    4'b0100: ACC <= {ACC[6:0], ACC[7]}; // CIL
                    4'b0101: ACC <= {1'b1, ACC[7:1]}; // ASR
                    4'b0110: begin
                        ACC <= ACC + 1;
                        C_B <= (ACC == 8'hFF);
                    end
                    4'b0111: begin
                        ACC <= ACC - 1;
                        C_B <= (ACC == 8'h00);
                    end
                endcase
            endcase
        end
        4'b0001, 4'b0010, 4'b0101, 4'b0110, 4'b0011, 4'b0111: begin
            ACC <= alu_out;

```

```

        EXT <= ext_out;
        C_B <= alu_CB;
    end
    4'b1001: ACC <= reg_data; // MOV ACC, Ri
    4'b1010: begin
        write_enable <= 1;
        write_reg <= reg_addr;
    end
    4'b1000: if (C_B == 1) PC <= reg_addr; // BR addr
    4'b1011: PC <= reg_addr; // RET addr
    4'b1111: PC <= PC; // HLT
endcase
if (opcode != 4'b1111 && !(opcode == 4'b1000 && C_B == 1) && opcode != 4'b1011)
    PC <= PC + 1;
end
end
endmodule

```

### Simulation testbench:

```

module TinyProcessor_tb;

    reg clk;
    reg reset;

    // Instantiate the processor
    TinyProcessor uut (
        .clk(clk),
        .reset(reset)
    );

    // Clock generation
    always #5 clk = ~clk; // 10ns clock period

    initial begin
        clk = 0; reset = 1;
        #1;

    // Preload values
        uut.rf.regs[0] = 8'd10;
        uut.rf.regs[1] = 8'd5;   // R1
        uut.rf.regs[2] = 8'd20;
        uut.rf.regs[3] = 8'd30;
        uut.rf.regs[4] = 8'd40;
        uut.rf.regs[5] = 8'd13;  // R5
        uut.rf.regs[6] = 8'd9;   // R6
    end
endmodule

```

```
uut.rf.regs[7] = 8'd0; // R7
uut.rf.regs[8] = 8'd80;
uut.rf.regs[9] = 8'd90;
uut.rf.regs[10] = 8'd100;
uut.rf.regs[11] = 8'd110;
uut.rf.regs[12] = 8'd120;
uut.rf.regs[13] = 8'd130;
uut.rf.regs[14] = 8'd140;
uut.rf.regs[15] = 8'd150;
```

#### // Program 1

```
uut.rom.ROM[0] = 8'b1001_0001; // MOV ACC, R1
uut.rom.ROM[1] = 8'b0110_0001; // XRA R1 (clears ACC)
uut.rom.ROM[2] = 8'b0001_0101; // ADD R5
uut.rom.ROM[3] = 8'b0010_0110; // SUB R6
uut.rom.ROM[4] = 8'b0011_1010; // MUL R10
uut.rom.ROM[5] = 8'b0101_0011; // AND R3
uut.rom.ROM[6] = 8'b0111_0100; // CMP R4
uut.rom.ROM[7] = 8'b0000_0001; // LSL
uut.rom.ROM[8] = 8'b0000_0010; // LSR
uut.rom.ROM[9] = 8'b0000_0011; // CIR
uut.rom.ROM[10] = 8'b0000_0100; // CIL
uut.rom.ROM[11] = 8'b0000_0101; // ASR
uut.rom.ROM[12] = 8'b0000_0110; // INC
uut.rom.ROM[13] = 8'b0000_0111; // DEC
uut.rom.ROM[14] = 8'b1010_0111; // MOV R7, ACC
uut.rom.ROM[15] = 8'b1111_1111; // HLT
```

#### // Program 2

```
// uut.rom.ROM[0] = 8'b1001_0001; // MOV ACC, R1
// uut.rom.ROM[1] = 8'b0110_0001; // XRA R1 (clears ACC)
// uut.rom.ROM[2] = 8'b0001_0101; // ADD R5
// uut.rom.ROM[3] = 8'b1011_0110; // RETURN TO 6
// uut.rom.ROM[4] = 8'b0011_1010; // MUL R10
// uut.rom.ROM[5] = 8'b0101_0011; // AND R3
// uut.rom.ROM[6] = 8'b0111_0100; // CMP R4
// uut.rom.ROM[7] = 8'b1000_1101; // BRANCH TO 13
// uut.rom.ROM[8] = 8'b0000_0010; // LSR
// uut.rom.ROM[9] = 8'b0000_0011; // CIR
// uut.rom.ROM[10] = 8'b0000_0100; // CIL
// uut.rom.ROM[11] = 8'b0000_0101; // ASR
// uut.rom.ROM[12] = 8'b0000_0110; // INC
// uut.rom.ROM[13] = 8'b0000_0111; // DEC
// uut.rom.ROM[14] = 8'b1010_0111; // MOV R7, ACC
// uut.rom.ROM[15] = 8'b1111_1111; // HLT
```

#### // Program 3

```
// uut.rom.ROM[0] = 8'b1001_0101; // MOV ACC, R5
```

```
// uut.rom.ROM[1] = 8'b0001_0110; // ADD R6
// uut.rom.ROM[2] = 8'b1010_0111; // MOV R7, ACC
// uut.rom.ROM[3] = 8'b1111_1111; // HLT
```

```
#15; reset = 0;
```

```
#200; $finish();
end
```

```
endmodule
```

### Simulation result:

#### Testing all operations:

##### Program 1:

##### Control flow:

**MOV ACC, R1** – Load the contents of register R1 into ACC.

**XRA R1** – XOR ACC with R1; this clears ACC if R1 equals itself.

**ADD R5** – Add the value of R5 to ACC.

**SUB R6** – Subtract the value of R6 from ACC.

**MUL R10** – Multiply ACC with the value in R10.

**AND R3** – Perform a bitwise AND between ACC and R3.

**CMP R4** – Compare ACC with R4; sets flags, no change to ACC.

**LSL** – Logical shift left; multiply ACC by 2.

**LSR** – Logical shift right; divide ACC by 2.

**CIR** – Circular shift right; rotates bits of ACC right.

**CIL** – Circular shift left; rotates bits of ACC left.


**ASR** – Arithmetic shift right; shifts right while preserving sign.

**INC** – Increment ACC by 1.

**DEC** – Decrement ACC by 1.

**MOV R7, ACC** – Copy the contents of ACC into register R7.

**HLT** – Halt the program execution.

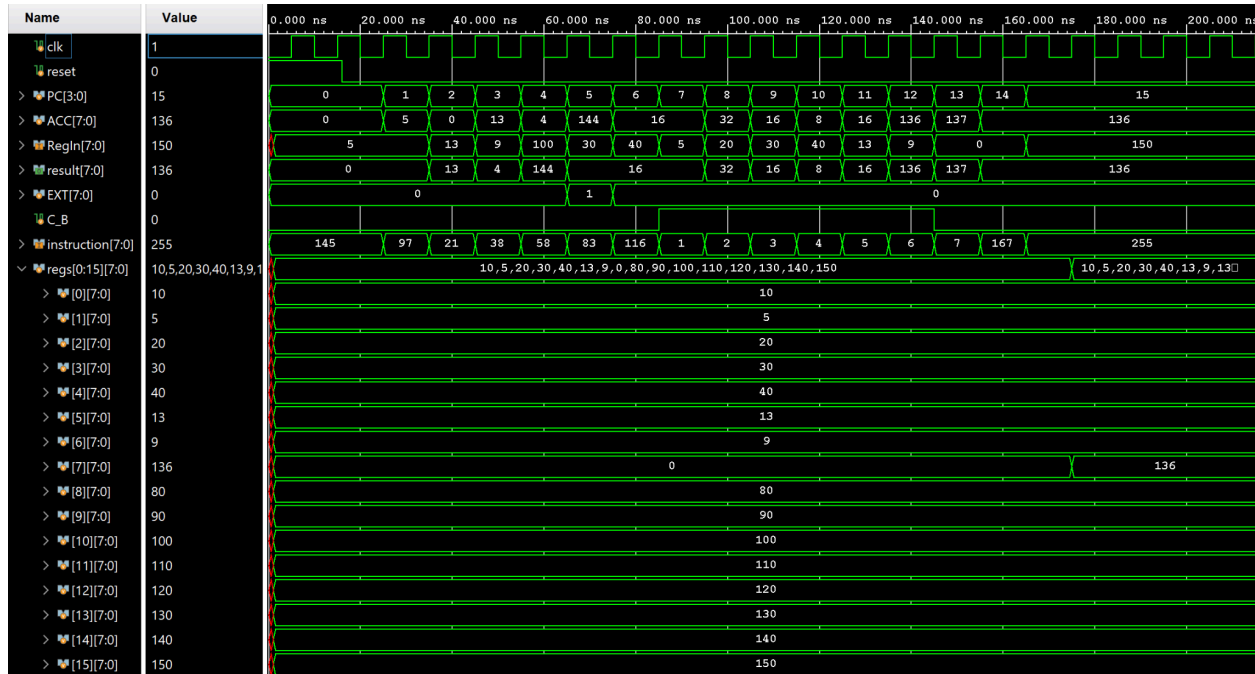

## Program 2:

### Control flow:

**MOV ACC, R1** – Load the contents of register R1 into ACC.

**XRA R1** – This would have cleared ACC if not commented.

**ADD R5** – Add the value in R5 to ACC.

**RET 6** – Return to instruction at address 6.

**MUL R10** – Skipped due to the return instruction.

**AND R3** – Skipped due to the return instruction.

**CMP R4** – Compare ACC with R4; flags updated, ACC unchanged.

**BR 13** – Branch to instruction at address 13.

**LSR** – Skipped due to branch.

**CIR** – Skipped due to branch.

**CIL** – Skipped due to branch.


**ASR** – Skipped due to branch.

**INC** – Skipped due to branch.

**DEC** – Decrement ACC by 1.

**MOV R7, ACC** – Store the current value of ACC into register R7.

**HLT** – Halt execution.

 

### Program 3: Sample code

Add the contents of R5 and R6, and store the result in R7.

